



Click to view this week's ad screen



[Ideas For Design]

Voltage-To-Current Converter Works From A Single-Supply Rail


R. Jayapal

ED Online ID #2985

February 17, 2003

Copyright © 2006 Penton Media, Inc., All rights reserved.

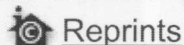Printing of this document is for personal use only.



Voltage-to-current converters feeding to grounded loads often find their way into industrial measurements and control applications. The conventional textbook circuit needs both positive and negative-supply rails (*Fig. 1*). In this circuit:

$$e_{in} - e_1 = I_L R_S$$

Therefore, the load current is:

$$I_L = e_{in}/R_S - e_1/R_S$$

The first term is proportional to the input voltage e_{in} , and the second term is a constant. Here, e_1 is derived from the negative power-supply rail through a potentiometer:

$$I_L = e_{in}/R_S + (-e_1)/R_S$$

R_S is selected so that the first term gives 16 mA for full-scale input voltage, and the potentiometer is adjusted so that the second term provides a constant 4 mA. In effect, the output ranges from 4 to 20 mA, corresponding with zero to full input voltage. But failure of the negative power supply causes erroneous output. Moreover, there may be equipment where the negative power supply is not available, requiring generation just for this

In such cases, there's a slightly different circuit that works on a single-supply rail (*Fig. 2*). This circuit uses one half of the quad operational LM324. The first amplifier is configured as a subtractor, while the second amplifier is configured as a current converter.

The output of the first amplifier at A equals e_1 minus e_{in} . Here, e_1 is derived from the positive power supply by potentiometer P_1 . The voltage equals V minus $I_L R_S$.

Symphony™ 24-Bit Audio DSPs

It's how you deliver better sound everywhere.

(Roll over stars to learn more)

New Symphony Studio Development Software. Learn more >

free

ENGINEERING TV

Sponsored by

NATIONAL INSTRUMENTS & ANALOG DEVICES

View Video


Op amp inputs at A and B are the same, so:

$$e_1 - e_{in} = V - I_L R_S$$

$$I_L = e_{in}/R_S + (V - e_1)/R_S$$


The first term is proportional to the input voltage, with the second term a constant. R_S is chosen so that the first term gives 16 mA for full voltage, and the potentiometer is adjusted such that the second term supplies a constant 4 mA. In effect, the output is 4 to 20 mA, correct zero to full input voltage. Thus, this circuit works without using a negative power-supply rail. For the circuit shown in Figure 2, the current is 4 to 20 mA with an input of 0 to 1 V.

Figure 1

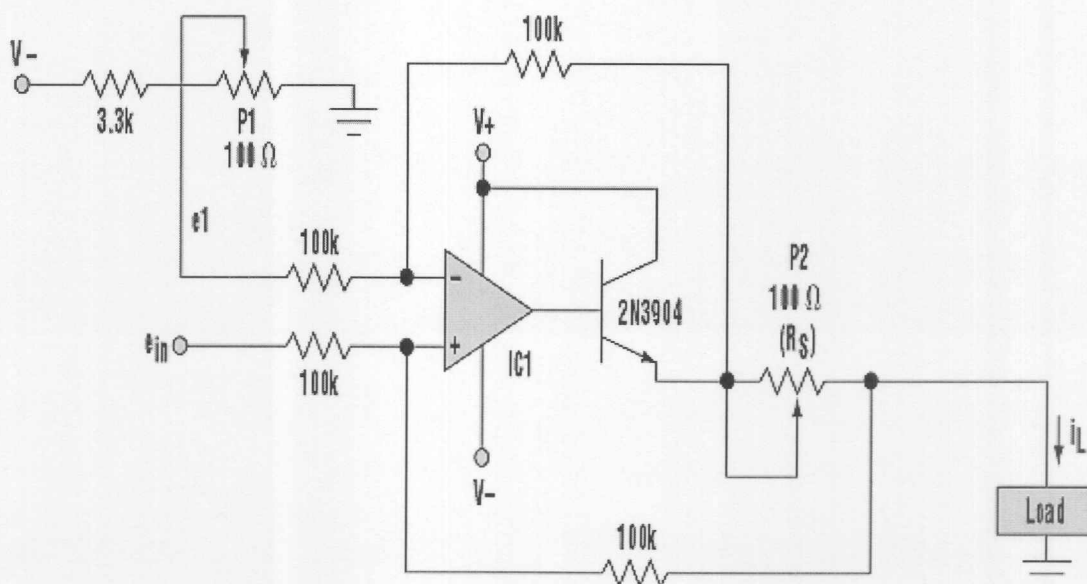

1. This conventional circuit gives 4 to 20 mA of output for an input of 0 to 1 V. First adjust P1 for zero (4 mA), then P2 for span (20 mA). The circuit needs a positive and a negative supply. Typical power supply voltages are ± 15 V.

Figure 2

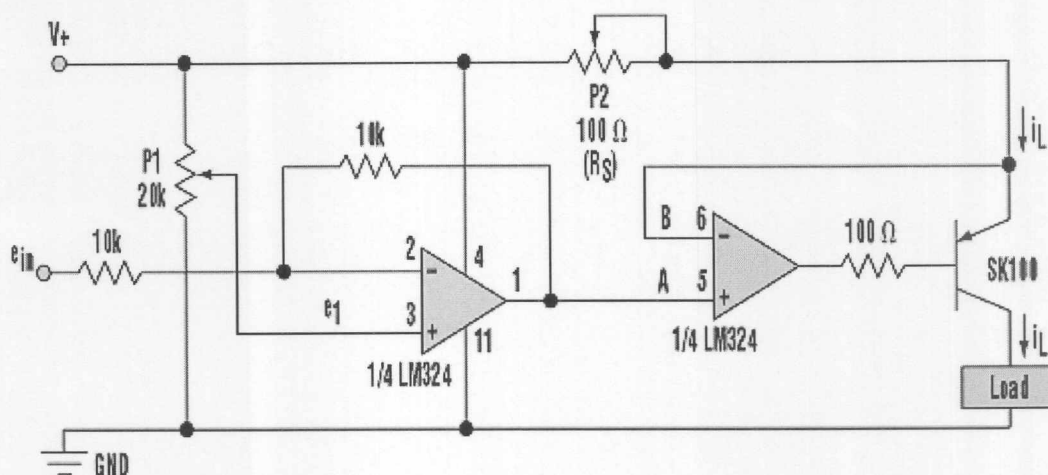

2. An alternate circuit provides between 4 and 20 mA of output corresponding to 0- to 1-V input. It uses only a positive supply (typical $V^+ = 15$ V). Adjust P1 for zero (4 mA) and P2 for span (20 mA). Load resistance can reach 500 Ω without saturation. Replace the transistor with a Darlington pair to reduce signal inaccuracy caused by the transistor's base current.

PartFinder



Find real-time pricing, stock status, same-day/next-day shipping options and more. Brought to you by **Digi-Key**. [Go to PartFinder](#).

Marketplace

Resolve the battle of performance vs. battery life

You don't have to choose between performance or battery life for your portable media player design. Freescale i.MX multimedia processors and Power Management ICs deliver on performance while maximizing battery life. Visit freescale.com/mobileconsumer

There will be 16 complimentary Seminars held between October 3 and November 8 2007 across US / Canada. Seats are limited, so for more information please call 1800-544-4186 or register today!

Design without prototype! How much time and money would you save? Join the Altium Designer Revolution and discover how Altium Designer allows you to develop, test, debug and interact live with your design without the need to construct development prototypes

Power Electronics Technology Exhibition & Conference Oct. 30-Nov.1, Dallas, TX

The power electronics industry's leading information event - find the right technologies, products and components to integrate into an ever-evolving array of complex applications.

Engineering TV: Videos for Electronic and Machine Design Engineers

Don't just read about the latest in engineering technology - see it in action on Engineering TV! Don't miss an episode.

Keithley Instruments -

Achieving Accurate and Reliable Resistance Measurements in Low Power and Low Voltage Applications.

Sponsored Links

Test Equipment Sale
Nolatek Equipment Closeout
Reduced
www.nolatek.com

RF & Microwave Power An
RF Amplifier Design and Ma
100KHz to 3 GHz. Custom /
www.nptrf.com


Industrial automation
30 years of engineering exp
system solution
www.techtrix.ca/frame1.html

USB 2.0 Controllers
Connect two PCs or periphe
Semiconductor hardware an
www.plxtech.com

Switch-Mode Power
Digital Power Tech, News, V
Conferences, Columns, Feat
www.PowerPulse.net



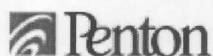Electronic Design Europe ■■■ Electronic Design China ■■■ EEPN ■■■ Power Electronics ■■■ Auto Electronics ■■■ Microwaves & RF ■
Schematics ■■■ Find Power Products ■■■ Military Electronics ■■■ Featured Vendors ■■■ EE Events ■■■ Free Design Resou



[Planet EE Network](#) | [Contact Us](#) | [Editorial Calendar](#) | [Media Kit](#) | [Submit Articles](#) | [Headlines](#) | [Site Feedback](#) | [Subscribe](#)

[Advanced Search](#) | [Help](#) | [Site Map](#)

Copyright © 2007 Penton Media, Inc., All rights reserved. [Privacy](#)